

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

Supplementary – Summer 2023

Course: B. Tech. Branch: Electronics & Telecommunication Engineering

Semester: III

Subject Code & Name: BTEXC302 Analog Circuits

Max Marks: 60

Date: 10/08/2023

Duration: 3Hr.

Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

	(Level/CO)	Marks
Q.1 Solve Any Two of the following.		12
A) Describe the block diagram of an operational amplifier (OP-AMP) and its main components.	Level 1	6
B) Explain the working principle of a differential amplifier.	Level 1	6
C) Discuss the need for level shifters in electronic circuits and explore the different types of level shifters commonly used.	Level 2	6
Q.2 Solve Any Two of the following.		12
A) Explain the working principle and circuit configuration of an integrator amplifier.	Level 3	6
B) Calculate the output voltage of an inverting amplifier with a gain of -5 when the input voltage is 2V.	Level 2	6
C) Describe the circuit of a summing amplifier and how it can add multiple input signals together.	Level 1	6
Q.3 Solve Any Two of the following.		12
A) How does a square wave generator circuit work? Describe a circuit that can generate a square wave output from a sine wave input.	Level 1	6
B) What is the need for precision rectifiers? Explain the challenges faced when rectifying low-level signals and how precision rectifiers overcome these issues.	Level 1	6
C) Explain the working principle of a triangular wave generator.	Level 2	6
Q.4 Solve Any Two of the following.		12
A) Describe the concept of a voltage-to-frequency (V-F) converter. How does it convert an input voltage into a corresponding frequency output?	Level 1	6
B) Explain the operation and design of a voltage-to-current (V-I) converter.	Level 1	6
C) Explain the working principle of a single slope analog-to-digital converter (ADC)	Level 1	6

- Q. 5 Solve Any Two of the following.** **12**
- A) Explain the working principle of RC oscillators. Describe the design of a phase-shift oscillator **Level 1** **6**
- B) Explain the operation of a Colpitts oscillator. **Level 2** **6**
- C) Explain the principle of oscillators and how they generate periodic waveforms. **Level 1** **6**

***** End *****