

Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

Level/(CO) Marks

Q. 1) Solve Any Two of the following.


12

A) What is BJT? Explain in detail.

1/7 6

B) Determine V_{CE} for the voltage divider bias configuration?

1/3 6

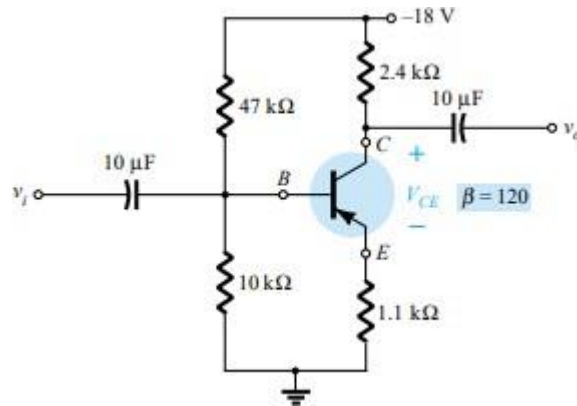

C) Draw a neat diagram of cascaded amplifier and explain in detail.

1/3 6

Q. 2) Solve Any Two of the following.

12


A) Explain construction & characteristics of JFET.

2/1 6

B) Determine the following parameter for given figure

2/1 6

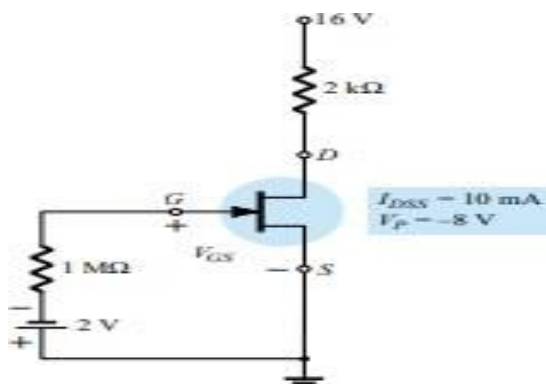- (a) V_{GSQ} .
- (b) I_{DQ} .
- (c) V_{DS} .
- (d) V_D .
- (e) V_G .
- (f) V_S .



C) Write short notes on CMOS.	1/5	6
Q. 3) Solve Any Two of the following.		12
A) Write short note on Transformer coupled class A power amplifier.	1/5	6
B) Derive Expression for Maximum Efficiency of Class B Power Amplifier?	2/1	6
C) Calculate the efficiency of a class B amplifier for a supply voltage of $V_{CC} = 24\text{ V}$ with peak output voltages of: (a) $V_L(p) = 22\text{ V}$. (b) $V_L(p) = 6\text{ V}$.	1/1	6
Q. 4) Solve Any Two of the following.		12
A) What is feedback? Explain its types in detail.	2/1	6
B) Determine the voltage gain, input, and output impedance with feedback for voltage series feedback having $A = -100$, $R_i = 10\text{ k}\Omega$, $R_o = 20\text{ k}\Omega$ for feedback of (a) $\beta = -0.1$ and (b) $\beta = -0.5$	1/7	6
C) Explain feedback amplifier in detail.	2/3	6
Q. 5) Solve Any Two of the following.		12
A) Explain RC phase shift oscillator in detail.	1/1	6
B) The tuned collector oscillator circuit used in the local oscillator of a radio receiver makes use of an LC tuned circuit with $L = 58.6\text{ }\mu\text{H}$ and $C = 300\text{ pF}$. Calculate the frequency of oscillations.	2/5	6
C) Write short note on Colpitts oscillator.	2/5	6

*** End ***