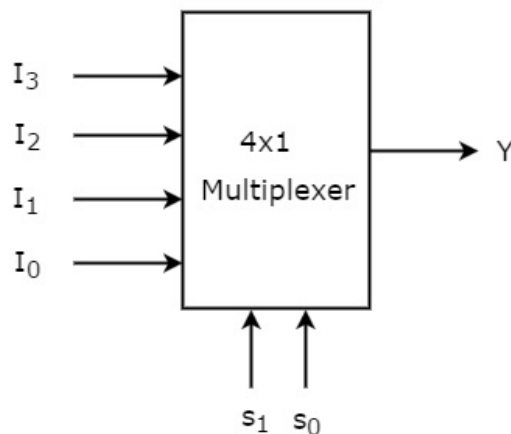


Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

	Level/(CO)	Marks
Q. 1) Solve Any Two of the following.		12
A) Minimize the following Boolean function- $F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$	CO1	6
B) For the given multiplexer circuit, determine the logic function?	CO2	6



C) Express the Boolean function $F = x + yz$ as a sum of minterms.	CO1	6
Q.2) Solve Any Two of the following.		12
A) Write short note on toggle flip flop.	CO3	6
B) Explain JK flip flop in detail.	CO2	6
C) Design 4 bit serial-in-parallel -out shift register is initially set to 1111. Data 1010 is applied to the input. After 3 clock pulses output will be	CO2	6
Q. 3) Solve Any Two of the following.		12
A) Implement a full adder circuit using a 3-to-8-line decoder.	CO1	6
B) Write short note on Mealy and Moore Type Finite State Machines	CO3	6

C) Explain ECL in detail.	C03	6
Q.4) Solve Any Two of the following.		12
A) Explain Operation of TTL NAND gate.	CO3	6
B) What are the important characteristics of digital ICs?	CO4	6
C) Compare the performance of TTL, CMOS and ECL Logic?	CO3	6
Q. 5) Solve Any Two of the following.		12
A) Explain General Architecture of FPGA in detail.	CO4	6
B) Write a short note on PAL & PLA.	CO3	6
C) What is VHDL? Explain in detail.	CO4	6

***** End *****