

| <p align="center">DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE</p> <p align="center">Supplementary Summer-2023</p> <p>Course: B. Tech. Branch: Electronics and Communication Engineering (Sandwich)</p> <p>Semester: III Subject Code & Name : Electronic Devices & Circuits (BTEXC303)</p> <p>Max Marks: 60 Date: 14/08/2023 Duration: 2:00 To 5:00 PM</p> | | | |
|---|--|------------|-----------|
| <p>Instructions to the Students:</p> <ol style="list-style-type: none"> 1. All the questions are compulsory. 2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question. 3. Use of non-programmable scientific calculators is allowed. 4. Assume suitable data wherever necessary and mention it clearly. | | | |
| | | Level/(CO) | Marks |
| Q. 1 | Solve Any Two of the following. | | 12 |
| A) | Explain E-MOSFET in detail. | C01 | 6 |
| B) | Write difference between JFET and MOSFET. | C03 | 6 |
| C) | Explain Construction and Characteristics of JFET. | C03 | 6 |
| Q.2 | Solve Any Two of the following. | | 12 |
| A) | Explain CMOS inverter in detail. | C02 | 6 |
| B) | Explain types of MOSFET. | C01 | 6 |
| C) | Explain D-MOSFET transfer characteristics. | C03 | 6 |
| Q.3 | Solve Any Two of the following. | | 12 |
| A) | Write classification of power amplifier. | CO2 | 6 |
| B) | Write advantages of negative feedback in feedback amplifier. | CO2 | 6 |
| C) | What are the four different types of feedback amplifier? Explain in detail | CO1 | 6 |
| Q.4 | Solve Any Two of the following. | | 12 |
| A) | State Barkhausen criterion for sustained oscillation. | CO1 | 6 |
| B) | Calculate a)operating frequency b) feedback fraction for Hartley oscillator Assume L1=1000uH L2=100uH M=20uH C=20pF | C03 | 6 |
| C) | In phase shift oscillator R1=R2=R3=1 MΩ C1=C2=C3=68pF at what frequency does the circuit oscillate? | C03 | 6 |
| Q.5 | Solve Any Two of the following. | | 12 |
| A) | Draw and Explain IC555 Block diagram. | C01 | 6 |
| B) | Explain A stable and Monostable multivibrator. | CO2 | 6 |
| C) | Write short note on “SMPS” | C03 | 6 |