	DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSIT	Y, LONERE				
	Winter Examination – 2022					
	Course: B. Tech. Branch : Electronics and Computer Engineering	Semester : III				
	Subject Code & Name: BTESC305 & Digital Electronics and Microprocessor					
	Max Marks: 60M Date: 17/03/2023 Durat	tion: 03:00 Hr.				
	 Instructions to the Students: All the questions are compulsory. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question. Use of non-programmable scientific calculators is allowed. Assume suitable data wherever necessary and mention it clearly. 					
0.1		(Level/CO)	Marks			
Q. 1	Solve Any Two of the following.		12M			
A)	Perform following Conversion. a. $(11100111)_2 = (?)_{gray}$ b. $(1792.12)_{10} = (?)_2$ c. $(338.025)_{10} = (?)_8$	BL2 & CO1	6			
B)	Explain the working of following gates with their truth table and logic diagram.	BL2 & CO1	6			
C)	Write a short note on multiplexer and demultiplexer.	BL2 & CO1	6			
Q.2	Solve Any Two of the following.		12M			
A)	Minimize the following equation using K-map.	BL3& CO2	6			
	a. $Y = \Sigma m(0,2,4,7,8,9,11,12,13)$					
	b. $Y = \Pi M(0,1,2,3,5,7)$					
B)	Explain the working of full substractor with truth table. Implement it with half substractor.	BL2& CO2	6			
C)	Design 2 bit digital comparator using logic gates.	BL3& CO2	6			
Q. 3	Solve Any Two of the following.		12M			
A)	Explain S-R flip flop with logic diagram and truth table.	BL3& CO3	6			
B)	What is counter? Explain 4-bit ring counter using D-flip flop. Implement its	BL2& CO3	6			
	truth table.					
C)	Write a short note on shift register and list down its application.	BL3& CO3	6			
Q.4	Solve Any Two of the following.		12M			
A)	Draw and explain block diagram of 8086 microprocessor and explain in detail.	BL1& CO4	6			
B)	Explain the addressing modes of 8086 with suitable example.	BL2& CO4	6			
C)	Explain the structure of 8086 PSW	BL3& CO4	6			

Q. 5	Solve Any Two of the following.		12M		
A)	Explain with example arithmetic group of instruction set in 8085.	BL3& CO5	6		
B)	Compare 8085 with 8086.	BL3& CO5	6		
C)	Write a program addition of two 16 bit number using 8085	BL3& CO5	6		
*** End ***					