

Figure 5

Q. 3 Solve Any One of the following.

- A)** In the network shown in figure 6 , the switch K is moved from position a to b at $t=0$. A steady state current being previously established , derive the expression for the current $i(t)$ using laplace transform.

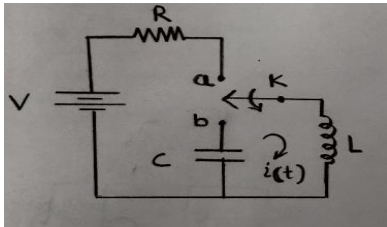


Figure 6

- B)** For the circuit shown in figure 7 ,solve for $i(t)$ by using Laplace Transform with the switch k closed at $t=0$. Assume zero initial conditions

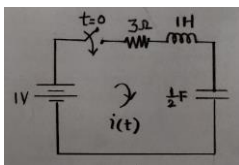


Figure 7

- C)** For the circuit shown in figure 8 find the current in 3Ω resistor using superposition theorem

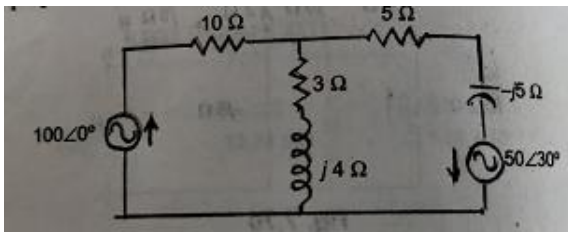


Figure 8

Q.4 Solve Any Two of the following.

- A)** Determine the short circuit admittance parameters for the network shown in figure 9

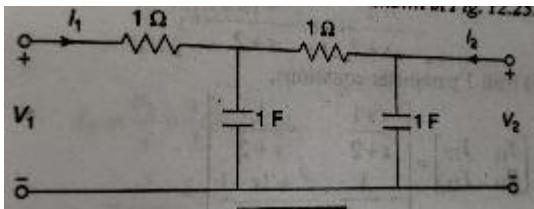


Figure 9

- B)** Determine the transmission parameters for thenetwork shown in figure10

CO3

6

CO3

6

CO1

6

CO4

6

CO4

6

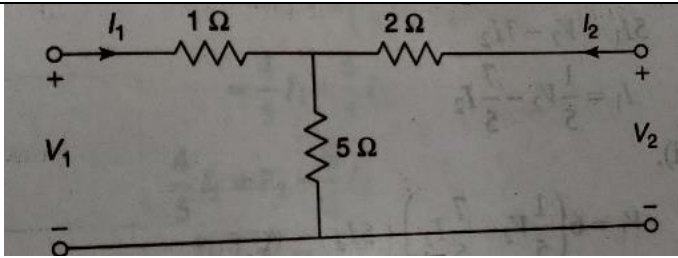


Figure 10

C) Determine the Z parameters for the network shown in figure 11

CO4

6

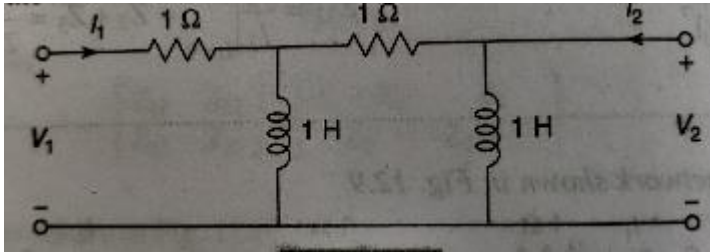


Figure 11

Q. 5 Solve Any One of the following.

A) Test the following polynomial for Hurwitz property

CO5

6

$$1.S^4+S^3+3S^2+2S+12$$

$$2.S^5+3S^3+2S$$

B) Realize the Foster I Form of the RC impedance function given below

CO5

6

$$Z(S)=[(S+1)(S+3)] / [S(S+2)]$$

C) Find the Cauer I Form of the RL impedance function given below

CO5

6

$$Z(S)=[2(S+1)(S+3)] / [(S+2)(S+6)]$$

*** End ***

The grid and the borders of the table will be hidden before final printing.