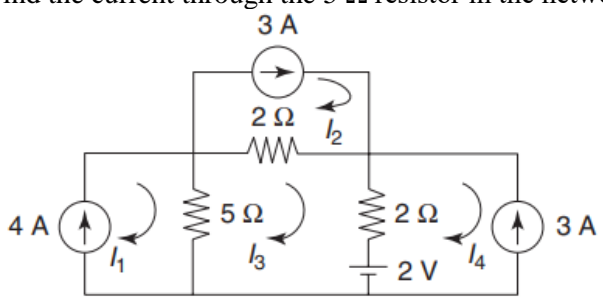
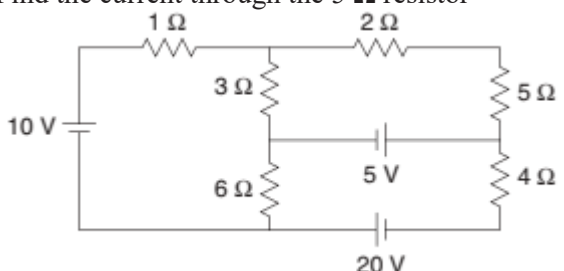
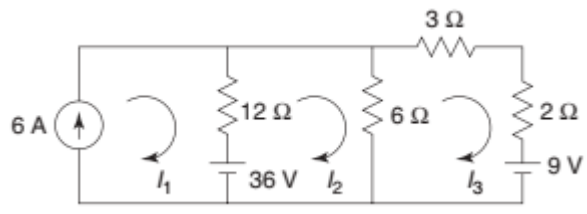
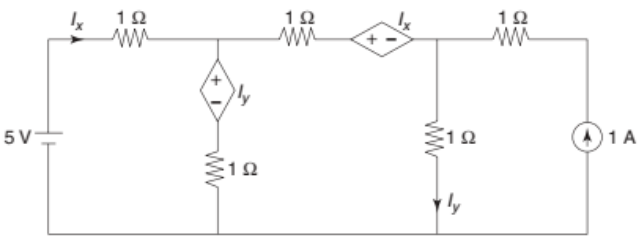
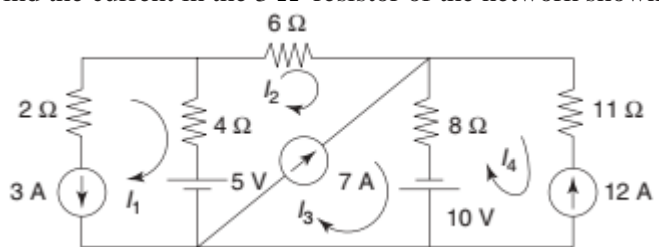
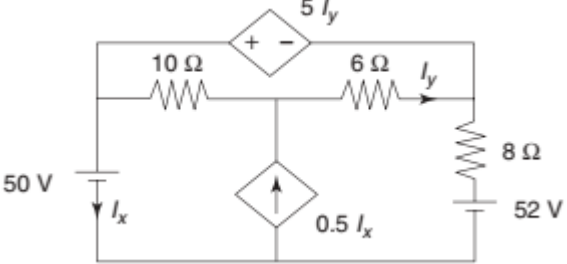
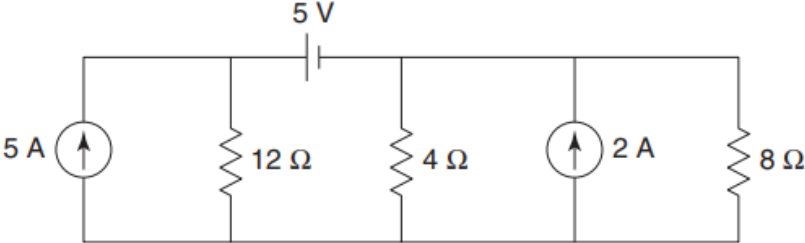
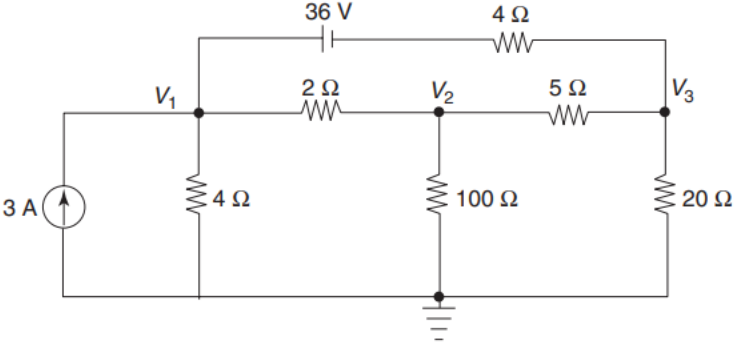
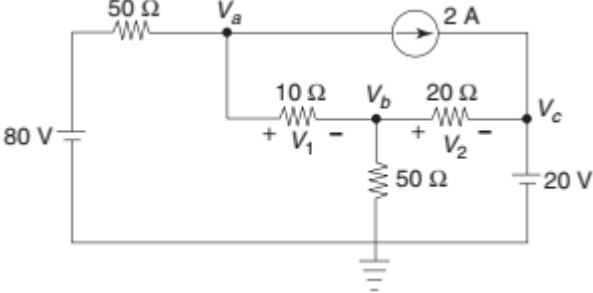
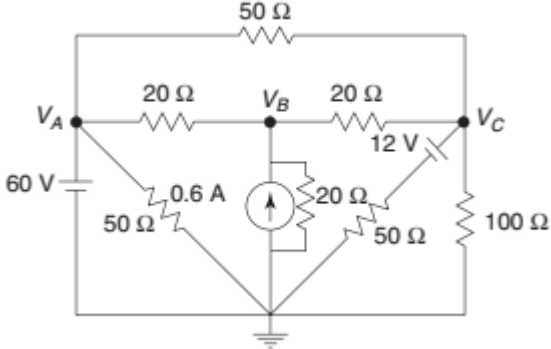


Question Bank for BTETC401 Network Theory

Unit- 1 (Network Theorems)

Sr.No	Questions
1	Define the terms: Network and Circuit, Linear and Non-linear Elements, Active and Passive Elements, Unilateral and Bilateral Elements, Lumped and Distributed Elements, Active and Passive Network, Time-invariant and Time-variant Network
2	State and explain Kirchoff's laws?
3	Mesh Analysis
i)	<p>Find the current through the 5 Ω resistor in the network of Fig</p> 
ii)	<p>Find the current through the 5 Ω resistor</p> 
iii)	<p>Find the current through the 2 ohm resistor in the network of Fig</p> 
iv)	<p>Find the currents in the three meshes of the network shown</p> 
v)	<p>Find the current in the 3 Ω resistor of the network shown</p> 

vi)	<p>find current through the 8 ohm resistor</p> 
4	<p>Explain the concept of source transformation? Find the current through the 8 Ω resistor in Fig.</p> 
5	<p>Node Analysis</p>
i)	<p>Determine the current through the 5 Ω resistor for the network shown in Fig.</p> 
ii)	<p>Find V_1 and V_2 for the network shown</p> 
iii)	<p>Find the voltage across the 100 Ω resistor for the network shown</p> 

iv) For the network shown in Fig, find the voltage V_x

v) For the network shown, find the node voltages V_1 and V_2 .

vi) find the node voltages

6 Maximum Power Transfer Theorem

i) What is the condition for maximum power transfer to the load?

ii) For the value of resistance R_L in Fig. for maximum power transfer and calculate the maximum power

iii) For the value of resistance R_L in Fig. for maximum power transfer and calculate the maximum power.







iv) For the network shown, find the value of R_L for maximum power transfer. Also, calculate maximum power.






v) Calculate the maximum power that may be dissipated in the load resistor R_L .

7 Thevenin's Theorem.

i) Find the current through the $20\ \Omega$ resistor in Fig

ii) Find the current through the $1\ \Omega$ resistor

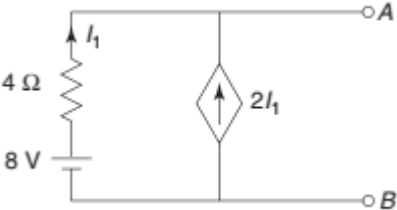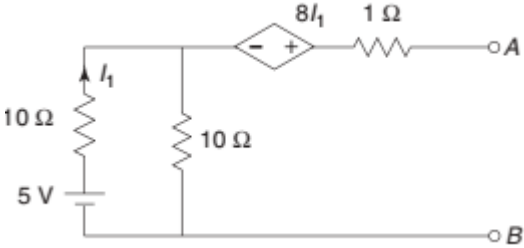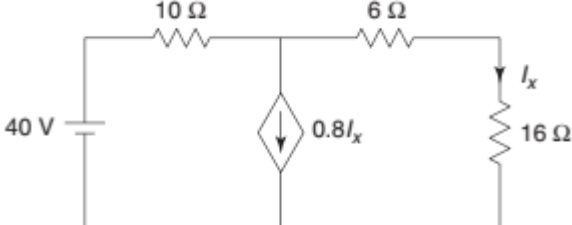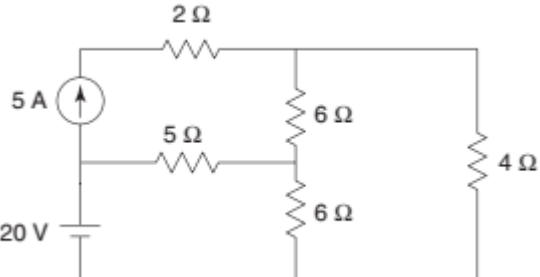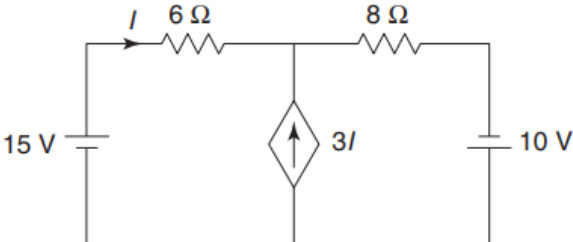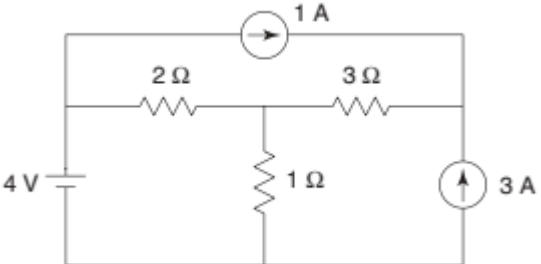iii)	<p>Obtain the Thevenin's equivalent network for the given network between terminal A and B</p> 
iv)	<p>Obtain the Thevenin's equivalent network for the given network between terminal A and B</p> 
v)	<p>Find the current in the 16 ohm resistor</p> 
8	<p>Superposition Theorem.</p>
i)	<p>Find the current through the 4 ohm resistor</p> 
ii)	<p>State and explain Superposition theorem? Find the current through the 6 ohm resistor</p> 
iii)	<p>Find the current in the 1 ohm resistors</p> 

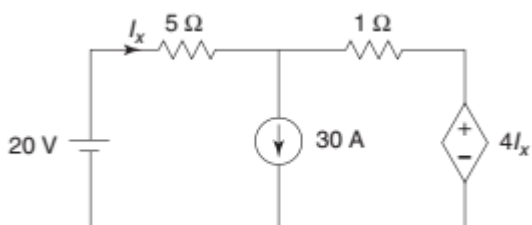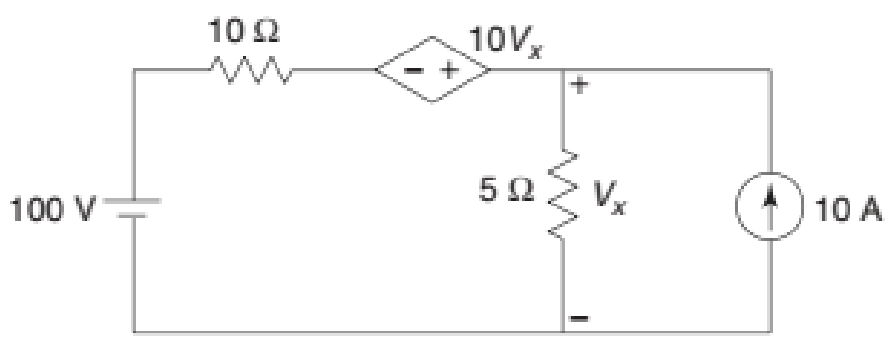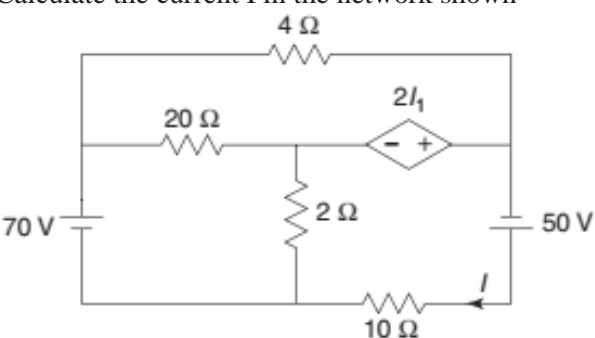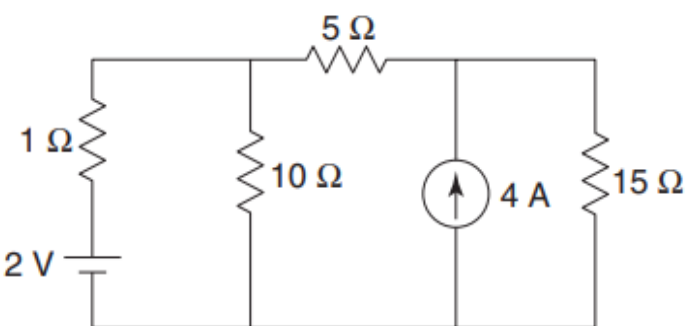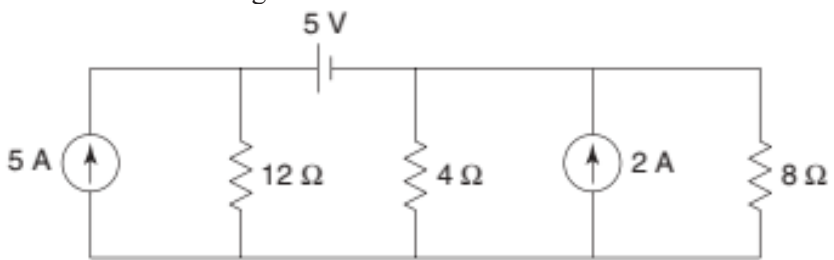iv)	<p>Find the current I_x</p> 
v)	<p>Determine the current through the $10\ \Omega$ resistor</p> 
vi)	<p>Calculate the current I in the network shown</p> 
9	Norton's Theorem
i)	State and explain Norton's theorem.
ii)	<p>Find the current through the $10\ \Omega$ resistor in Fig. Using Norton's theorem.</p> 
iii)	<p>Find the current through the $8\ \Omega$ resistor</p> 

iv) For the network shown in Fig., find Norton's equivalent network

v) Find Norton's equivalent network to the left of terminal A-B in Fig.





vi) Find Norton's equivalent network across terminals A and B

vii) Find the current through the 10 Ω resistor

10 **Graph Theory**


i) Define the following (i) Branch (ii) Sub graph (iii) Node (iii) Tree and co-tree (iv) Planar and non-Planar Graph (V) Loop or circuit

ii) For the graph shown below find incidence and cut set matrices.
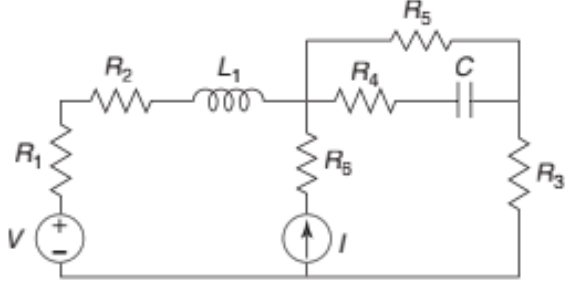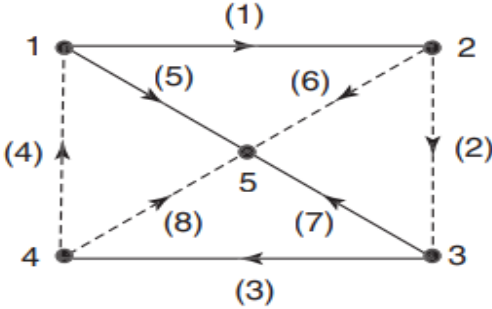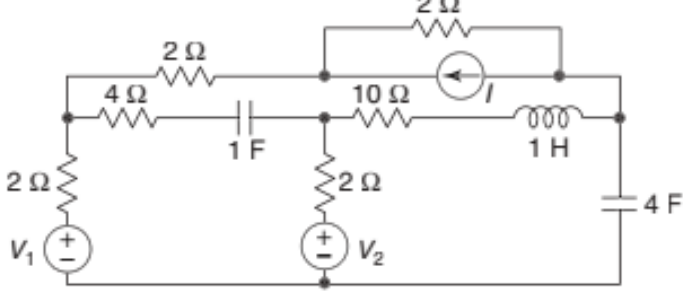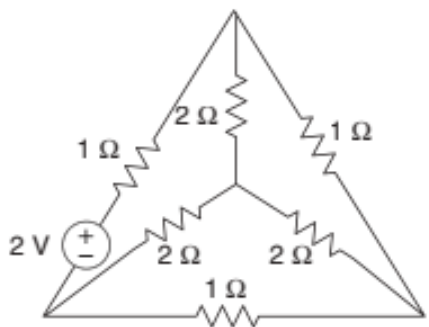
<p>iii)</p>	<p>For the circuit shown , draw the oriented graph and write the (a) incidence matrix, (b) tieset matrix, and (c) f-cutset matrix.</p> 
<p>iv)</p>	<p>For the graph shown in Fig. , write the incidence matrix, tieset matrix and f-cutset matrix</p> 
<p>v)</p>	<p>Draw the oriented graph and write the (a) incidence matrix, (b) tieset matrix, and (c) f-cutset matrix.</p> 
<p>vi)</p>	<p>The reduced incidence matrix of an oriented graph is</p> $A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$ <p>(a) Draw the graph. (b) How many trees are possible for this graph? (c) Write the Tieset and Cutset matrices</p>
<p>vii)</p>	<p>Write down the tieset matrix and obtain the network equilibrium equation in matrix form using KVL. Calculate the loop currents and branch currents.</p> 


viii)

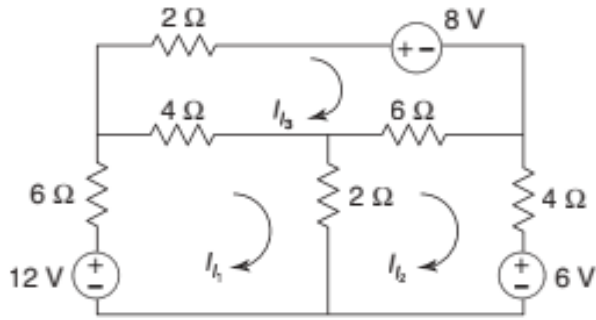Write down the tie-set matrix and obtain the network equilibrium equation in matrix form using KVL. Calculate loop currents













ix)





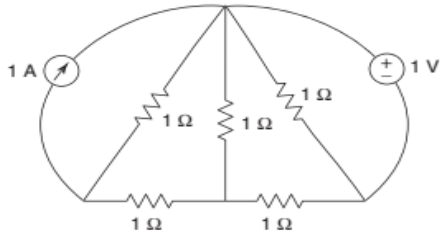
Draw the oriented graph. Write the tie-set schedule and hence obtain the equilibrium equation on loop basis. Calculate the values of branch currents and branch voltages.












Unit-2 (Transient Analysis and Frequency Domain Analysis)

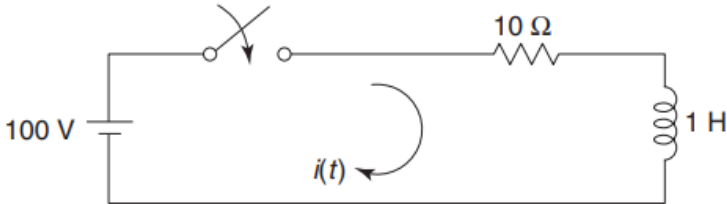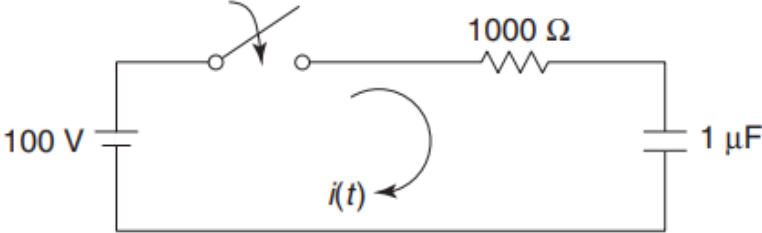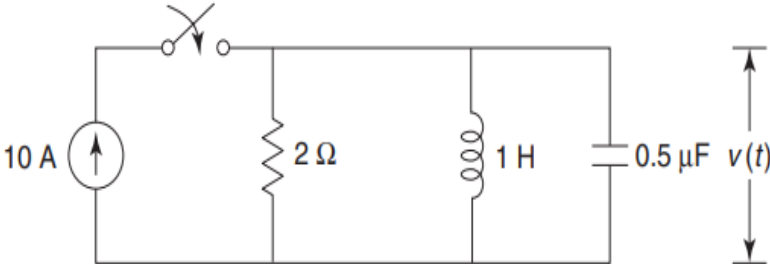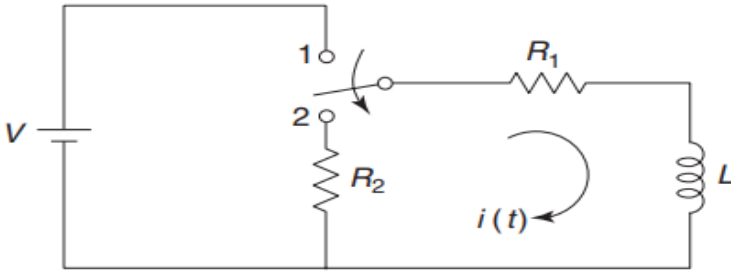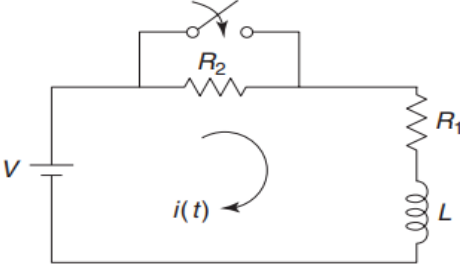Sr.No	Questions	
1	What are initial conditions? Explain the initial conditions for Resistor, capacitor and inductor.	
2	<p>In the given network of Fig., the switch is closed at $t = 0$. With zero current in the inductor, find i, di/dt and d^2i/dt^2 at $t = 0^+$.</p> 	
3	<p>In the network of Fig., the switch is closed at $t = 0$. With the capacitor uncharged, find value for I, di/dt and d^2i/dt^2 at $t = 0^+$.</p> 	
4	<p>For the network shown in Fig. , the switch is closed at $t = 0$, determine v, dv/dt and d^2v/dt^2 at $t = 0^+$.</p> 	
5	<p>In the network of Fig., the switch is initially at the position 1. On the steady state having reached, the switch is changed to the position 2. Find current $i(t)$.</p> 	
6	<p>In the network shown in Fig., the switch is closed at $t = 0$, a steady state having previously been attained. Find the current $i(t)$.</p> 	

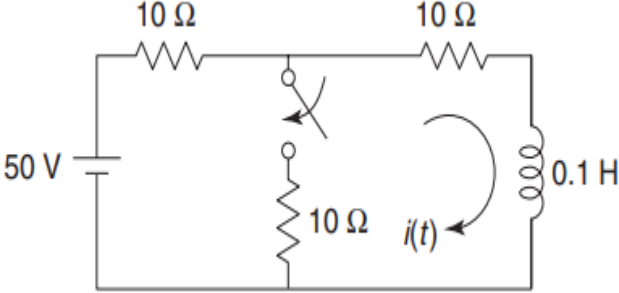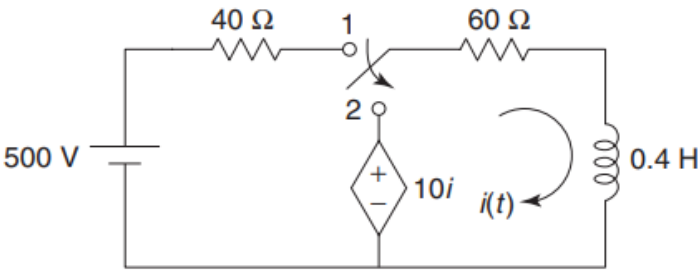
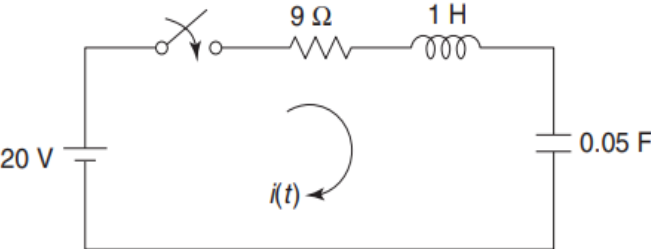
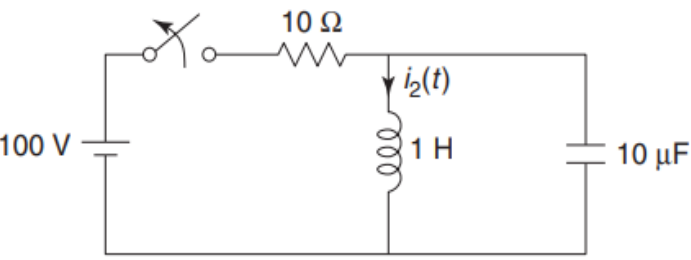
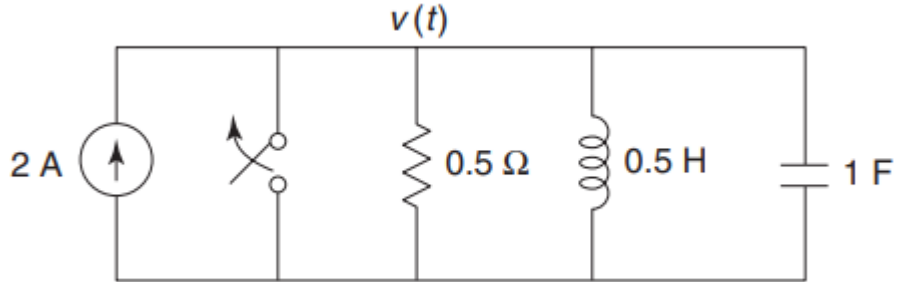
7	<p>In the network of Fig. , the switch is open for a long time and it closes at $t = 0$. Find $i(t)$.</p> 	
8	<p>For the network shown in Fig. , find the current $i(t)$ when the switch is changed from the position 1 to 2 at $t = 0$.</p> 	
9	<p>In the network of Fig. , the switch is closed at $t = 0$. Obtain the expression for current $i(t)$ for $t > 0$</p> 	
10	<p>In the network of Fig. , the switch is closed and a steady state is reached in the network. At $t = 0$, the switch is opened. Find the expression for the current $i_2(t)$ in the inductor.</p> 	
11	<p>In the network of Fig. , the switch is opened at $t = 0$ obtain the expression for $v(t)$. Assume zero initial conditions.</p> 	

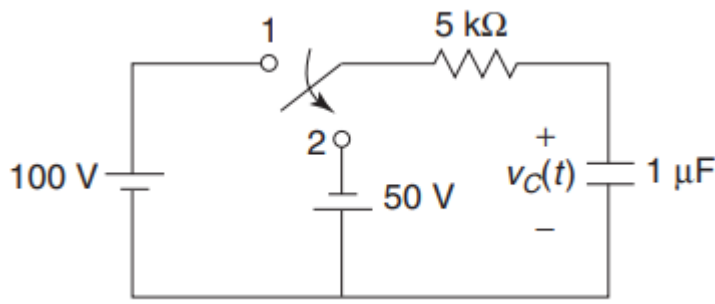
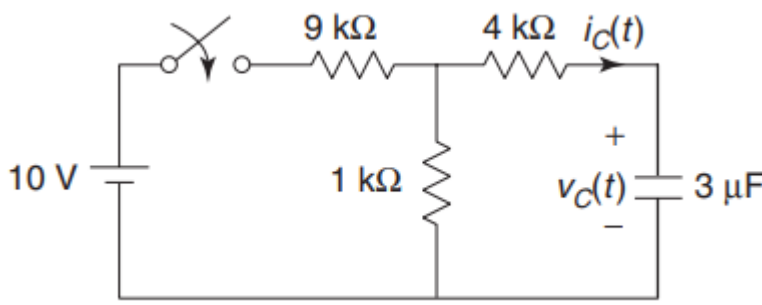
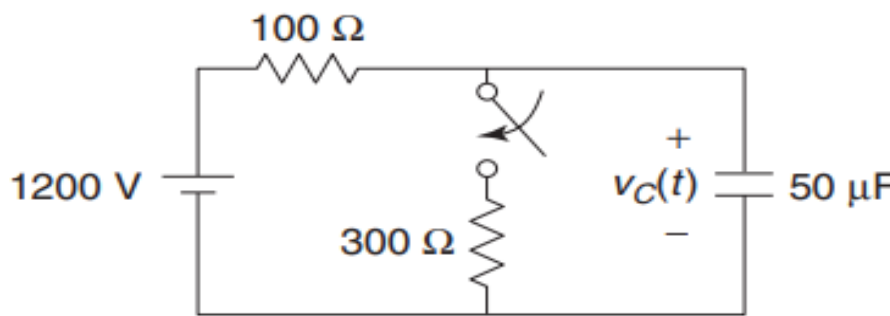
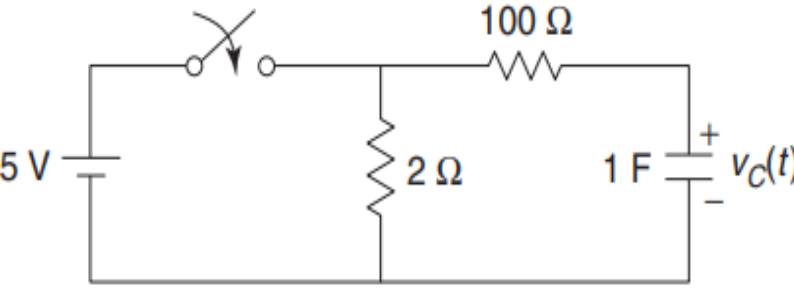
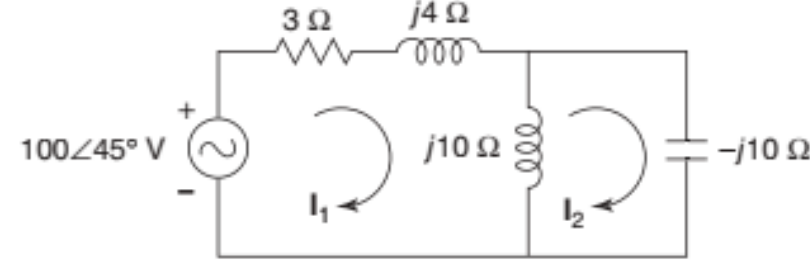
12	<p>The switch in the circuit of Fig. is moved from the position 1 to 2 at $t = 0$. Find $v_C(t)$</p> 	
13	<p>In the network shown in Fig., the switch closes at $t = 0$. The capacitor is initially uncharged. Find $v_C(t)$ and $i_C(t)$.</p> 	
14	<p>For the network shown in Fig. , the switch is open for a long time and closes at $t = 0$. Determine $v_C(t)$.</p> 	
15	<p>In Fig shown, the switch is closed at $t = 0$ Find $v_C(t)$ for $t > 0$.</p> 	
16	<p>Find mesh currents I_1 and I_2 in the network using Mesh Analysis</p> 	

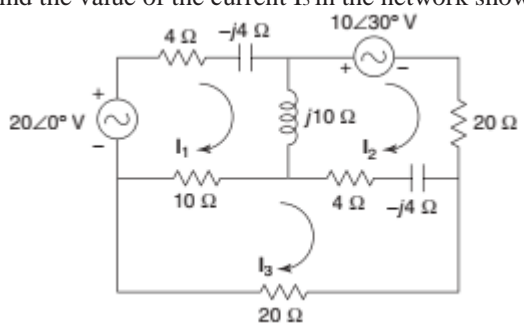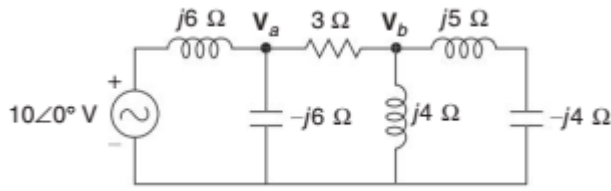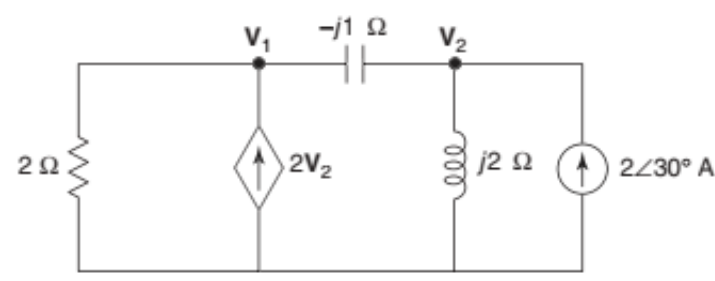
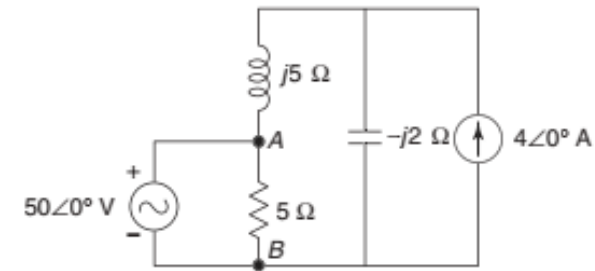
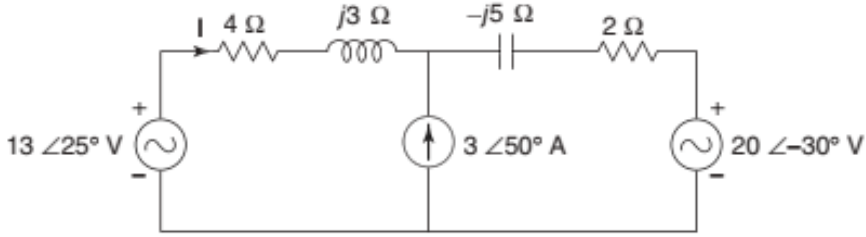
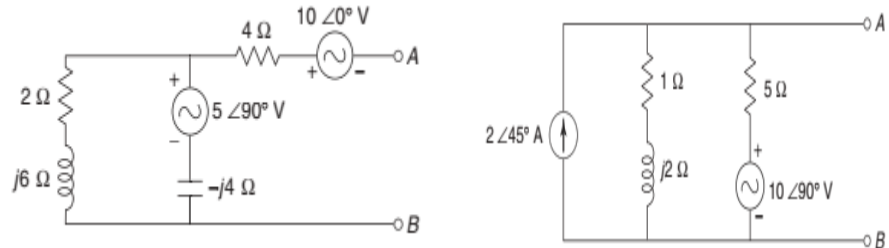
17	<p>Find the value of the current I_3 in the network shown</p> 	
18	<p>Determine V_a and V_b using node Analysis</p> 	
19	<p>Determine V_1 and V_2 using node Analysis</p> 	
20	<p>Determine the voltage V_{AB} for the network shown, using Superposition Theorem</p> 	
21	<p>Find the current I in the network using Superposition Theorem</p> 	
22	<p>Obtain Thevenin's equivalent network</p> 	

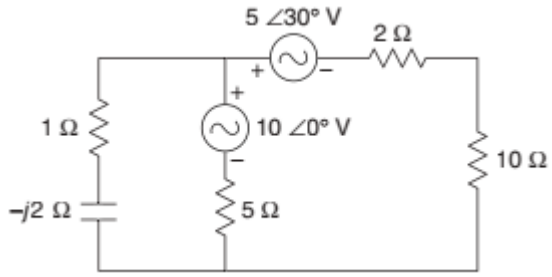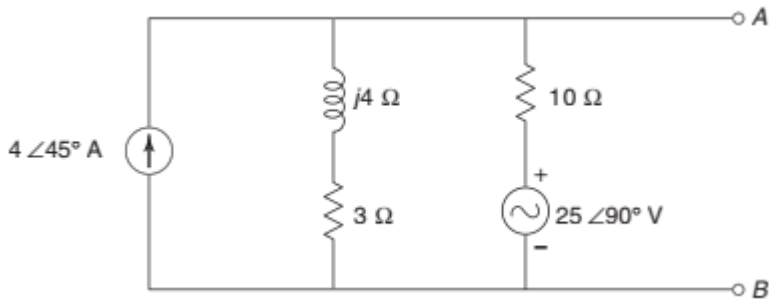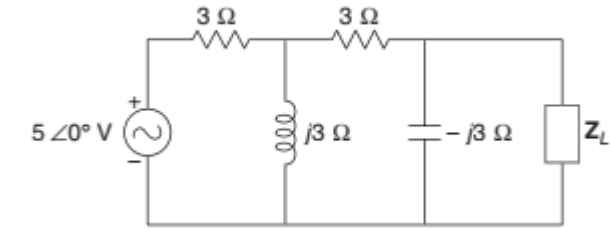23	<p>find the current through the $10\ \Omega$ resistor using Thevenin's theorem</p> 	
24	<p>Obtain Norton's equivalent network</p> 	
25	<p>Find the impedance Z_L so that maximum power can be transferred to it in the network of Figure shown. Find maximum power</p> 	





Unit-3 (Laplace transform and its circuit applications)


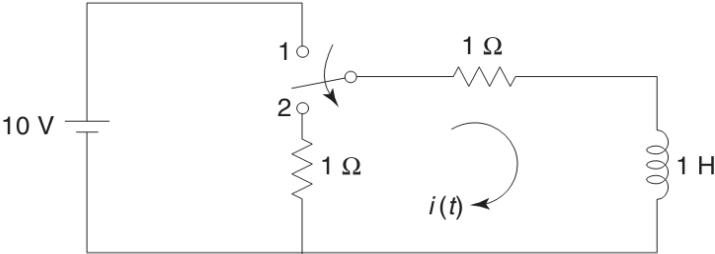
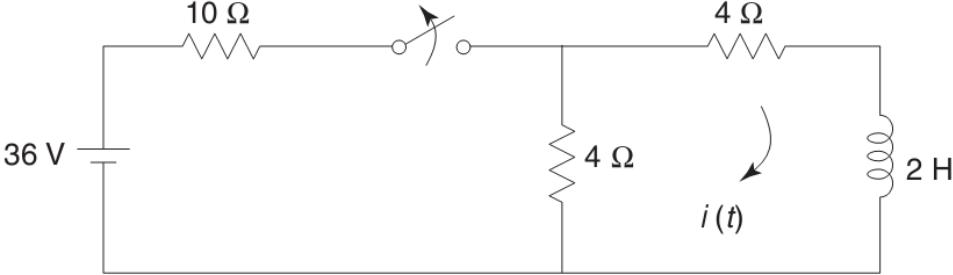
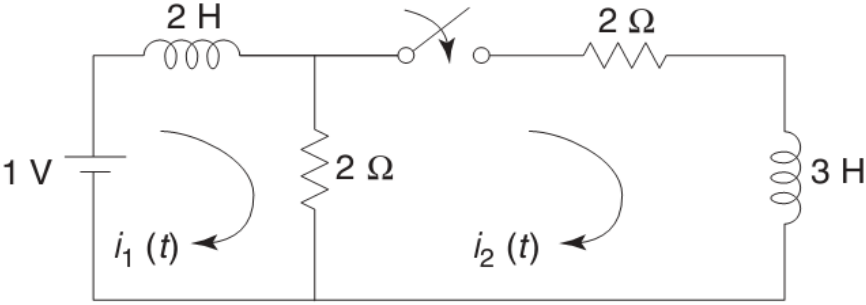
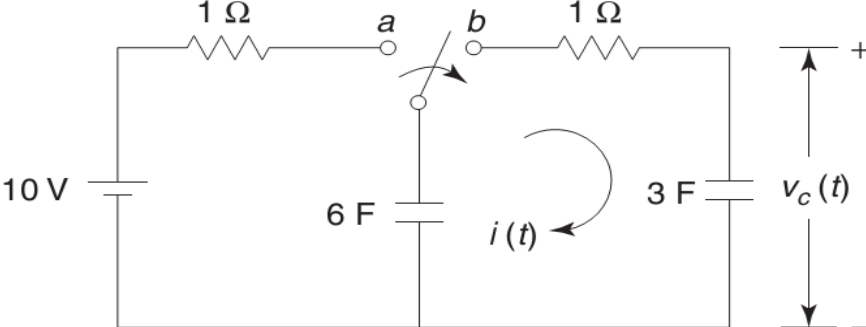
Sr.No	Questions
1	Derive Transient and steady state response of R-L, R-C , R-L-C circuit to various functions (i.e.with Unit step, Unit ramp and Unit impulse function)
2	Explain the Behaviour of basic elements in Laplace Transform
3	Find Laplace Transform of various standard time domain functions
4	<p>In the network of Fig. given below , the switch is moved from the position 1 to 2 at $t = 0$, steady-state condition having been established in the position 1. Determine $i(t)$ for $t > 0$.</p> 
5	<p>In the network of Fig. below, the switch is opened at $t = 0$. Find $i(t)$.</p> 
6	<p>In the network shown in Fig, the switch is closed at $t = 0$, the steady-state being reached before $t = 0$. Determine current through inductor of 3 H.</p> 
7	<p>In the network of Fig, the switch is closed at $t = 0$ with the network previously unenergised. Determine currents $i_1(t)$.</p> 

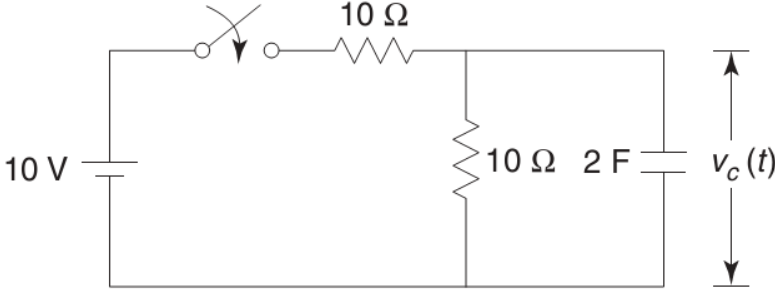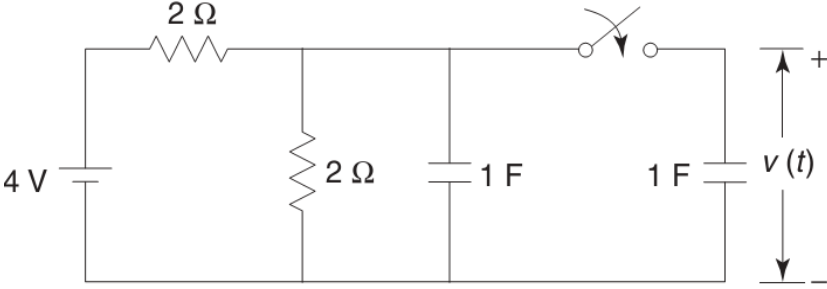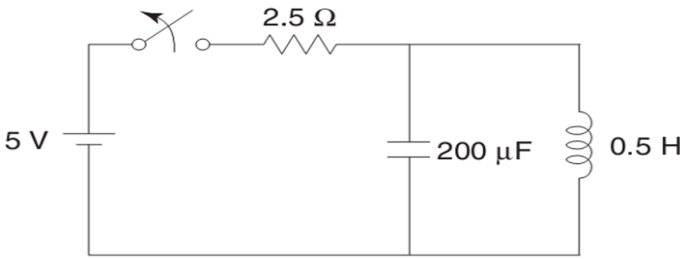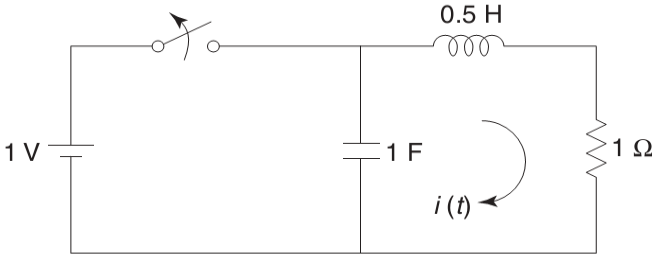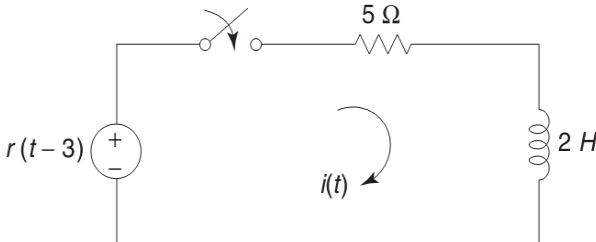8	<p>The switch in the network shown in Fig. is closed at $t = 0$. Determine the voltage across the capacitor</p> 
9	<p>The network shown in Fig. has acquired steady-state at $t < 0$ with the switch open. The switch is closed at $t = 0$. Determine $v(t)$.</p> 
10	<p>In the network of Fig, the switch is closed and steady-state is attained. At $t = 0$, switch is opened. Determine the current through the inductor</p> 
11	<p>In the network shown below, the switch is opened at $t = 0$. Steady-state condition is achieved before $t = 0$. Find $i(t)$.</p> 
12	<p>For the network shown below, determine the current $i(t)$ when the switch is closed at $t = 0$. Assume that initial current in the inductor is zero.</p> 

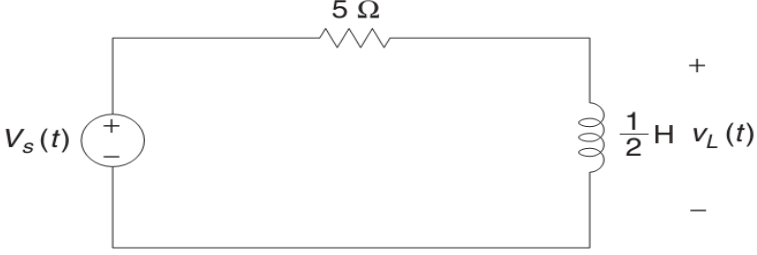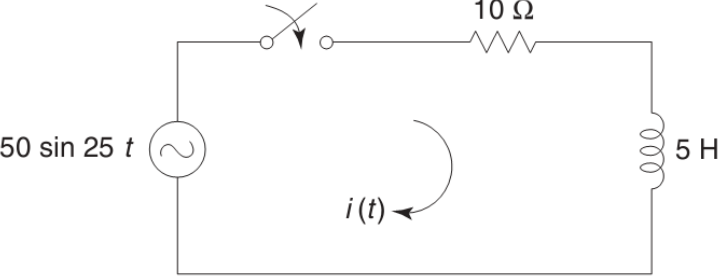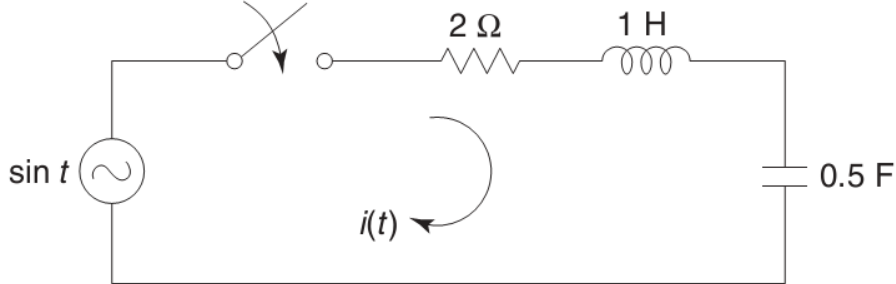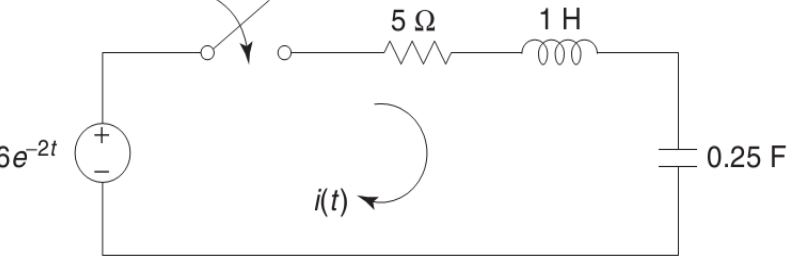13	<p>Determine the expression for $v_L(t)$ in the network shown. Find $v_L(t)$ when (i) $v_s(t) = \delta(t)$, and (ii) $v_s(t) = e^{-t} u(t)$.</p> 
14	<p>For the network shown, determine the current $i(t)$ when the switch is closed at $t = 0$.</p> 
15	<p>For the network shown, the switch is closed at $t = 0$. Determine the current $i(t)$ assuming zero initial conditions</p> 
16	 <p>For the network shown above, the switch is closed at $t = 0$. Determine the current $i(t)$ assuming zero initial conditions in the network elements</p>
17	<p>To find Initial and Final values if they exist of the signal with L.T.</p> $\frac{(S+10)}{S^2+3S+2} \quad \text{and} \quad \frac{S^2+5S+2}{S^2+3S+2}$


Unit-4 (Two Port Networks)

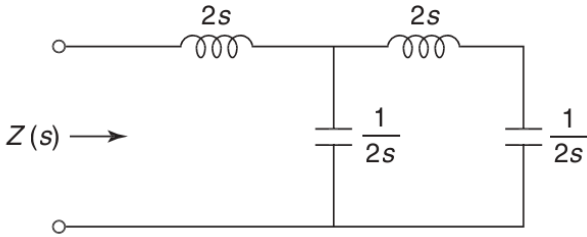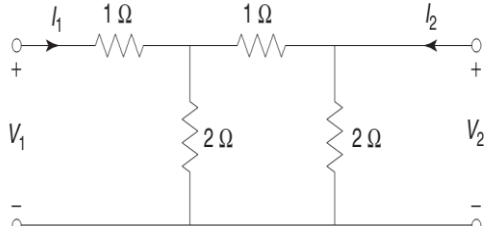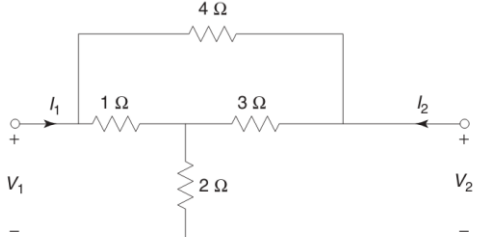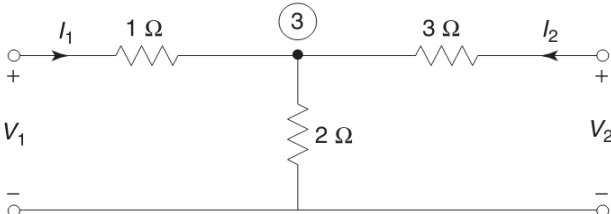Sr.No	Questions	
1	Define the term <ol style="list-style-type: none"> 1. Driving-point Impedance Function 2. Driving-point Admittance Function 3. Voltage Transfer Function 4. Current Transfer Function 5. Transfer Impedance Function 6. Transfer Admittance Function 	
2	Determine the driving-point impedance of the network shown <div style="text-align: center;">  </div>	
3	Find Z parameter for the network given below and Determine whether the network is symmetrical and reciprocal <div style="text-align: center;">  </div>	
4	Find the open-circuit impedance parameters for the network shown below. Determine whether the network is symmetrical and reciprocal <div style="text-align: center;">  </div>	
5	Find Y-parameters, h-parameter and Z-parameter and ABCD parameter for the network given below <div style="text-align: center;">  </div>	

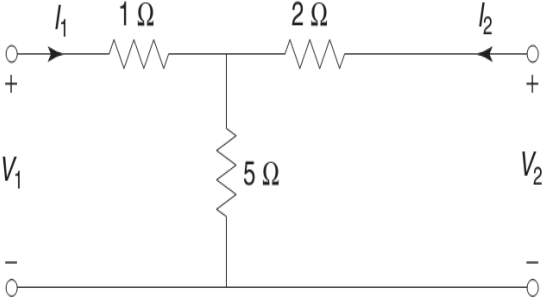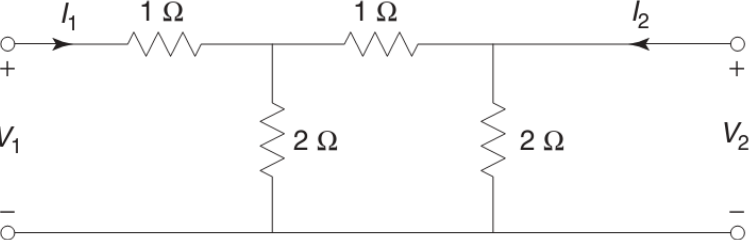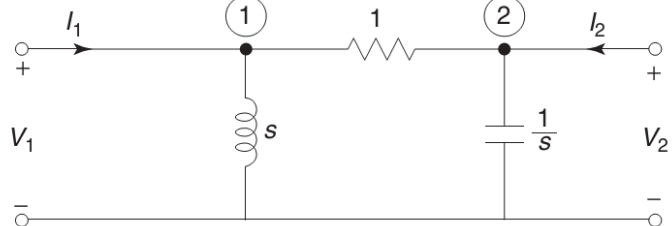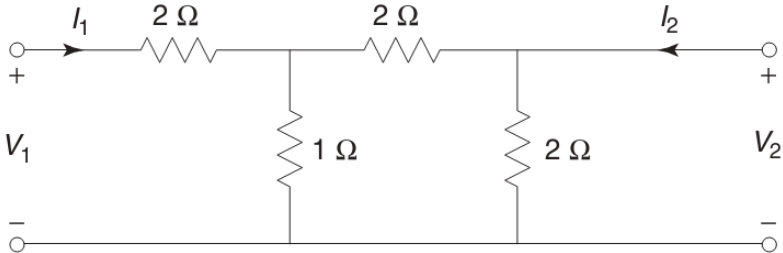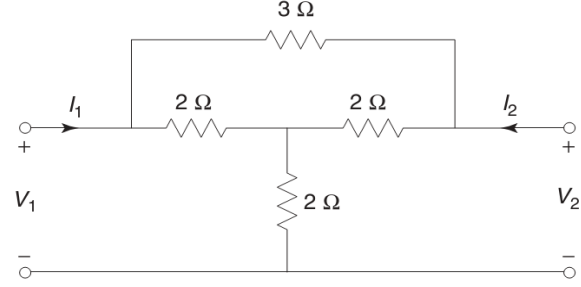6	<ul style="list-style-type: none"> • Derive Z parameter in terms of Y-parameter, h-parameter and ABCD parameter • Derive Y-parameter in terms of Z parameter, h-parameter and ABCD parameter • Derive h-parameter in terms of Z parameter, Y-parameter and ABCD parameter 	
7	<p>Find h-parameter, Y-parameters and Z-parameter and ABCD parameter for the network given below</p> 	
8	<p>Obtain ABCD parameters for the network shown</p> 	
9	<p>Determine the transmission parameters for the network shown</p> 	
10	<p>Determine hybrid parameters for the network shown. Determine whether the network is reciprocal.</p> 	
11	<p>Determine Y-parameters for the network shown</p> 	


12

Find Y-parameters for the network shown

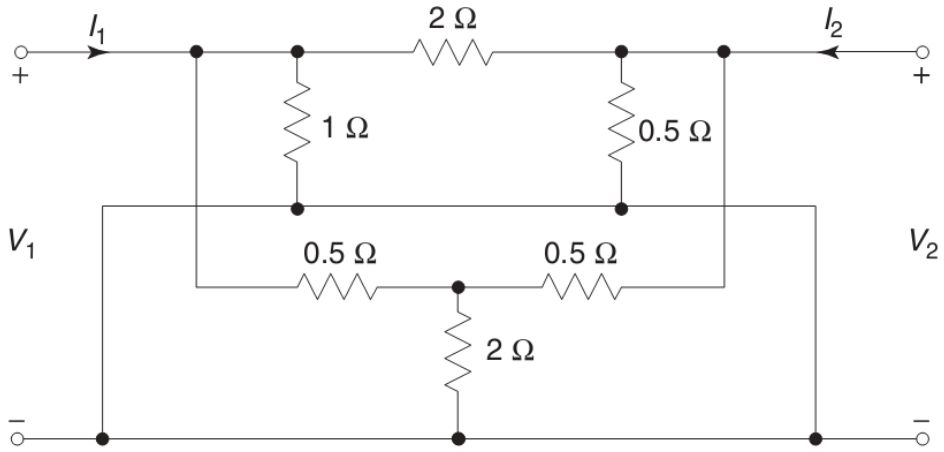


13

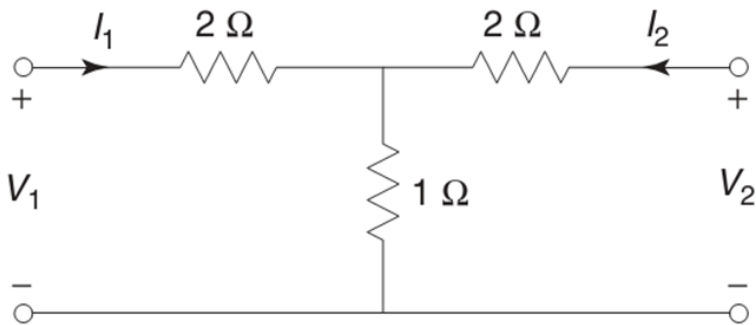Two identical sections of the network shown in Fig. are connected in series. Obtain Z-parameters of the overall connection









14

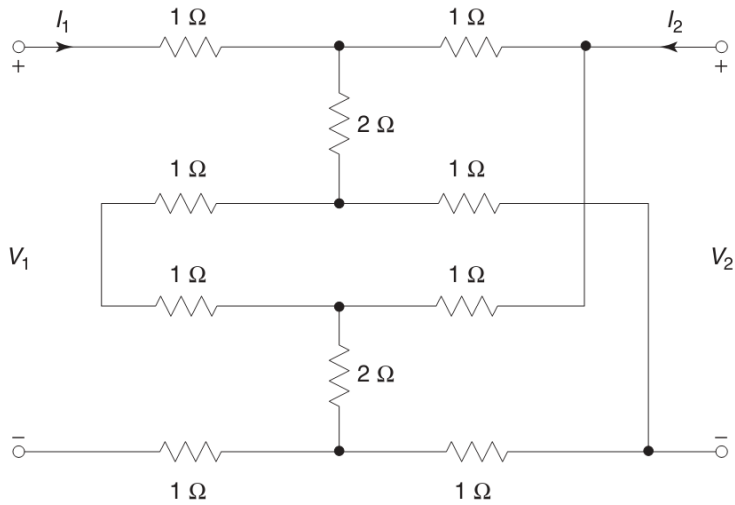Determine h-parameters for the network shown



Unit-5 (State Variable Analysis and RL & RC Network Synthesis)

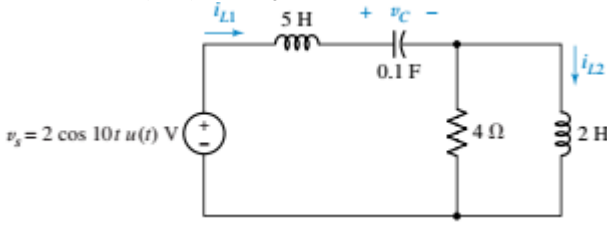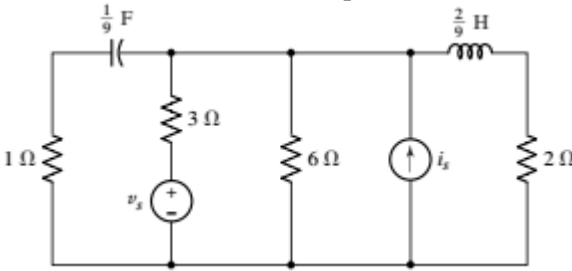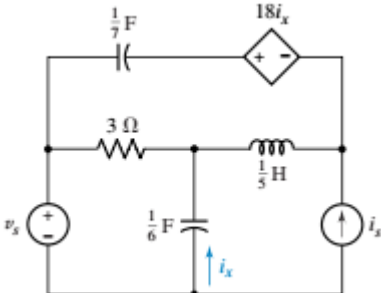Sr.No	Questions	
1	<p>Write a set of normal-form equations for the circuit shown in Fig, Order the state variables as i_{L1}, i_{L2}, and v_C.</p> 	
2	<p>Write a set of normal-form equations for the circuit of Fig shown</p> 	
3	<p>Find the set of normal-form equations for the circuit</p> 	
4	<p>Using the state vector $q = \begin{bmatrix} i \\ v \end{bmatrix}$, determine the system matrix and the forcing-function vector for the circuit of Fig. shown. (b) Repeat for the state vector $q = \begin{bmatrix} v \\ i \end{bmatrix}$</p>	
5	<p>a) Which of the following functions are L-C driving point impedances? Why?</p> $Z_1(s) = \frac{s(s^2 + 4)(s^2 + 16)}{(s^2 + 9)(s^2 + 25)}, \quad Z_2(s) = \frac{(s^2 + 1)(s^2 + 8)}{s(s^2 + 4)}$ <p>b) Synthesize the realizable impedances in a foster and cauer form</p>	
6	<p>Indicate which of the following functions are either R-C, R-L or L-C impedance functions</p> <p>(a) $Z(s) = \frac{s^3 + 2s}{s^4 + 4s^2 + 3}$</p> <p>(b) $Z(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$</p> <p>(c) $Z(s) = \frac{s^2 + 4s + 3}{s^2 + 6s + 8}$</p> <p>(d) $Z(s) = \frac{s^2 + 5s + 6}{s^2 + s}$</p> <p>(e) $Z(s) = \frac{s^4 + 5s^2 + 6}{s^3 + s}$</p>	

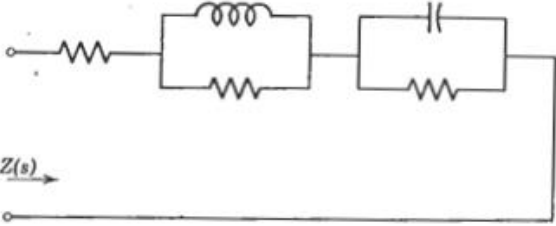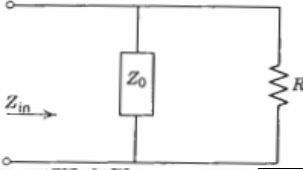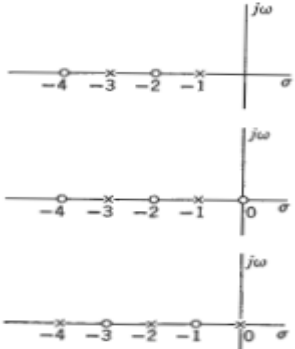7	<p>Synthesize $Z(s) = \frac{(s+2)(s+4)}{(s+1)(s+5)}$ into the form shown in the figure.</p>  <p style="text-align: center;">$Z(s)$ →</p>	
8	<p>The input impedance for network shown is,</p> $Z_{in} = \frac{2s^2 + 2}{s^3 + 2s^2 + 2s + 2}$ <p>If Z_0 is an L-C network: (a) Find the expression for Z_0. (b) Synthesize Z_0 in a Foster series form.</p> 	
9	<p>Synthesize the following functions in Cauer form.</p> $Z(s) = \frac{s^3 + 2s^2 + s + 1}{s^3 + s^2 + s}$ $Z(s) = \frac{s^3 + s^2 + 2s + 1}{s^4 + s^3 + 3s^2 + s + 1}$ $Z(s) = \frac{4s^3 + 3s^2 + 4s + 2}{2s^2 + s}$	
10	<p>Of the three pole-zero diagrams shown, pick the diagram that represents an R-L impedance function and synthesize in a series Foster form</p> 	
11	<p>a. Explain about classification of filters. Draw the characteristics of Low-pass and High-pass filters.</p> <p>b. Explain about Propagation constant and Characteristic impedance in Π-network filters and T-network filters.</p> <p>c. Explain about Constant-K low-pass filter, Constant-K high-pass filter, Constant-K band-pass filter in detail.</p>	
12	<p>A constant K low pass filter is designed to cut-off at a frequency of 1000Hz and the resistance of the load circuit is 50Ω. Calculate the values of the corresponding components required.</p>	
13	<p>Design a constant k low pass filter Π and T sections at a frequency of 5KHz and a design impedance of 1000Ω. Calculate the attenuation constant at a frequency of 6kHz and phase shift of 1kHz.</p>	

14	The elements of a T section of a constant K low pass filter are as shown Inductance=50m H each And Capacitance=0.01 μ F. calculate the cut-off frequency and characteristic impedances at a frequency of 1KHz and 5KHz. Also find the attenuation and phase shift at 1 kHz and 5 kHz.	
15	Design a constant k-high pass filter band pass filter to have a cut-off frequency of 2000Hz , 5000Hz , 2 KHz and a design impedance of 100 Ω .	