

BTINC603: Power Electronics & Drives

Chapter 1:

- 1) With the help of neat waveforms explain reverse recovery characteristics of Power Diode.
- 2) Discuss switching characteristics of Power BJT
- 3) With the help of neat waveforms explain characteristics of Power MOSFET
- 4) Discuss switching characteristics of Power MOSFET
- 5) Discuss switching characteristics of IGBT
- 6) Give the comparison between different types of power diodes
- 7) With the help of neat diagram explain working & requirements of general firing circuit

Chapter 2:

- 1) What is electrical drive? Draw a neat block diagram of electrical drive system & explain its different sections in brief.
- 2) Explain dynamic & steady state stability of an electrical drive system
- 3) Discuss in detail four quadrant operation of motor
- 4) Write a note on load equalization
- 5) Discuss in detail dynamics of electrical drive system

Chapter 3:

- 1) Define the terms semi converter, full converter, dual converter
- 2) With the help of neat circuit diagram explain operation of single-phase semi converter drive.
- 3) With the help of neat circuit diagram explain operation of single-phase full converter drive.
- 4) With the help of neat circuit diagram explain operation of single-phase dual converter drive.
- 5) With the help of neat circuit diagram explain operation of three phase semi converter drive.

- 6) With the help of neat circuit diagram explain operation of three phase full converter drive.
- 7) With the help of neat circuit diagram explain operation of three phase dual converter drive.
- 8) Discuss in detail closed loop control of DC drive

Chapter 4:

- 1) Draw a neat circuit diagram of single phase AC voltage control (ON-OFF control) & explain its operation with the help of neat waveforms
- 2) Draw a neat circuit diagram of single-phase AC voltage control (Phase control) & explain its operation with the help of neat waveforms
- 3) Draw a neat circuit diagram of single-phase Step-down AC voltage controller & explain its operation with the help of neat waveforms
- 4) Draw a neat circuit diagram of single-phase Step-Up AC voltage controller & explain its operation with the help of neat waveforms
- 5) Draw a neat circuit diagram of three phase Step-down AC voltage controller & explain its operation with the help of neat waveforms
- 6) Draw a neat circuit diagram of three phase Step-Up AC voltage controller & explain its operation with the help of neat waveforms
- 7) What is cyclo-converter? What are its types? List out its application
- 8) What is AC Voltage controller? What are its control techniques? List out its application

Chapter 5:

- 1) Explain starting, braking & Speed control of three phase induction motor
- 2) With the help of neat circuit diagram explain stator voltage control for speed control of induction motor drives
- 3) With the help of neat circuit diagram explain frequency control for speed control of induction motor drives
- 4) With the help of neat circuit diagram explain rotor voltage control for speed control of induction motor drives
- 5) With the help of neat circuit diagram explain voltage & frequency control for speed control of induction motor drives
- 6) Discuss in detail current control technique
- 7) Discuss in detail Multiquadrant operation of induction motor drives fed from Voltage Source Inverters

- 8) Write notes on Static Scherbius drive and Static Kramer drives
- 9) Explain in detail Static rotor resistance control method, static slip power recovery control-
- 10)

Chapter 6:

- 1) Explain any one technique of Speed control of Synchronous motor
- 2) Explain in detail adjustable frequency operation of synchronous motors
- 3) What are the different principles of synchronous motor control? Explain
- 4) Explain self-controlled synchronous motor drive using load commutated thyristor inverter
- 5) Discuss in detail voltage source inverter drive with open loop control
- 6) Explain self-controlled synchronous motor with electronic commutation
- 7) Explain closed loop speed control of Induction Motor